



Electric Circuits

Sixth Edition

500 fully solved problems


25 problem-solving videos online



USE WITH THESE COURSES

Electric Circuits • Electric Circuit Fundamentals • Electric Circuit Analysis • Linear Circuits and Systems • Circuit Theory

24.
G21.3192
M154
2014
-3

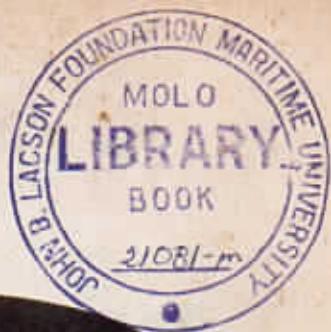

SCHAUM'S.
outlines

Electric Circuits

Sixth Edition

Mahmood Nahvi, PhD

*Professor Emeritus of Electrical Engineering
California Polytechnic State University*

Joseph A. Edminister

*Professor Emeritus of Electrical Engineering
The University of Akron*

Schaum's Outline Series



New York Chicago San Francisco Athens London Madrid
Mexico City Milan New Delhi Singapore Sydney Toronto

Contents

CHAPTER 1	Introduction	1
1.1	Electrical Quantities and SI Units	1.2 Force, Work, and Power
1.3	Electric Charge and Current	1.4 Electric Potential
	1.5 Energy and Electrical Power	1.6 Constant and Variable Functions
CHAPTER 2	Circuit Concepts	7
2.1	Passive and Active Elements	2.2 Sign Conventions
	2.3 Voltage-Current Relations	2.4 Resistance
	2.5 Inductance	2.6 Capacitance
	2.7 Circuit Diagrams	2.8 Nonlinear Resistors
CHAPTER 3	Circuit Laws	24
3.1	Introduction	3.2 Kirchhoff's Voltage Law
	3.3 Kirchhoff's Current Law	3.4 Circuit Elements in Series
	3.5 Circuit Elements in Parallel	3.6 Voltage Division
	3.7 Current Division	
CHAPTER 4	Analysis Methods	37
4.1	The Branch Current Method	4.2 The Mesh Current Method
	4.3 Matrices and Determinants	4.4 The Node Voltage Method
	4.5 Network Reduction	4.6 Input Resistance
	4.7 Output Resistance	4.8 Transfer Resistance
	4.9 Reciprocity Property	4.10 Superposition
	4.11 Thévenin's and Norton's Theorems	4.12 Maximum Power Transfer Theorem
	4.13 Two-Terminal Resistive Circuits and Devices	4.14 Interconnecting Two-Terminal Resistive Circuits
	4.15 Small-Signal Model of Nonlinear Resistive Devices	
CHAPTER 5	Amplifiers and Operational Amplifier Circuits	72
5.1	Amplifier Model	5.2 Feedback in Amplifier Circuits
	5.3 Operational Amplifiers	5.4 Analysis of Circuits Containing Ideal Op Amps
	5.5 Inverting Circuit	5.6 Summing Circuit
	5.7 Noninverting Circuit	5.8 Voltage Follower
	5.9 Differential and Difference Amplifiers	5.10 Circuits Containing Several Op Amps
	5.11 Integrator and Differentiator Circuits	5.12 Analog Computers
	5.13 Low-Pass Filter	5.14 Decibel (dB)
	5.15 Real Op Amps	5.16 A Simple Op Amp Model
	5.17 Comparator	5.18 Flash Analog-to-Digital Converter
	5.19 Summary of Feedback in Op Amp Circuits	

CHAPTER 6 Waveforms and Signals

117

- 6.1** Introduction **6.2** Periodic Functions **6.3** Sinusoidal Functions
6.4 Time Shift and Phase Shift **6.5** Combinations of Periodic Functions
6.6 The Average and Effective (RMS) Values **6.7** Nonperiodic Functions
6.8 The Unit Step Function **6.9** The Unit Impulse Function **6.10** The Exponential Function **6.11** Damped Sinusoids **6.12** Random Signals

CHAPTER 7 First-Order Circuits

143

- 7.1** Introduction **7.2** Capacitor Discharge in a Resistor **7.3** Establishing a DC Voltage Across a Capacitor **7.4** The Source-Free *RL* Circuit **7.5** Establishing a DC Current in an Inductor **7.6** The Exponential Function Revisited **7.7** Complex First-Order *RL* and *RC* Circuits **7.8** DC Steady State in Inductors and Capacitors **7.9** Transitions at Switching Time **7.10** Response of First-Order Circuits to a Pulse **7.11** Impulse Response of *RC* and *RL* Circuits **7.12** Summary of Step and Impulse Responses in *RC* and *RL* Circuits **7.13** Response of *RC* and *RL* Circuits to Sudden Exponential Excitations **7.14** Response of *RC* and *RL* Circuits to Sudden Sinusoidal Excitations **7.15** Summary of Forced Response in First-Order Circuits **7.16** First-Order Active Circuits

CHAPTER 8 Higher-Order Circuits and Complex Frequency

179

- 8.1** Introduction **8.2** Series *RLC* Circuit **8.3** Parallel *RLC* Circuit **8.4** Two-Mesh Circuit **8.5** Complex Frequency **8.6** Generalized Impedance (*R*, *L*, *C*) in *s*-Domain **8.7** Network Function and Pole-Zero Plots **8.8** The Forced Response **8.9** The Natural Response **8.10** Magnitude and Frequency Scaling **8.11** Higher-Order Active Circuits

CHAPTER 9 Sinusoidal Steady-State Circuit Analysis

209

- 9.1** Introduction **9.2** Element Responses **9.3** Phasors **9.4** Impedance and Admittance **9.5** Voltage and Current Division in the Frequency Domain **9.6** The Mesh Current Method **9.7** The Node Voltage Method **9.8** Thévenin's and Norton's Theorems **9.9** Superposition of AC Sources

CHAPTER 10 AC Power

237

- 10.1** Power in the Time Domain **10.2** Power in Sinusoidal Steady State **10.3** Average or Real Power **10.4** Reactive Power **10.5** Summary of AC Power in *R*, *L*, and *C* **10.6** Exchange of Energy between an Inductor and a Capacitor **10.7** Complex Power, Apparent Power, and Power Triangle **10.8** Parallel-Connected Networks **10.9** Power Factor Improvement **10.10** Maximum Power Transfer **10.11** Superposition of Average Powers

CHAPTER 11 Polyphase Circuits

266

- 11.1** Introduction **11.2** Two-Phase Systems **11.3** Three-Phase Systems **11.4** Wye and Delta Systems **11.5** Phasor Voltages **11.6** Balanced Delta-Connected Load **11.7** Balanced Four-Wire, Wye-Connected Load

11.8 Equivalent Y- and Δ -Connections	11.9 Single-Line Equivalent Circuit for Balanced Three-Phase Loads	11.10 Unbalanced Delta-Connected Load	11.11 Unbalanced Wye-Connected Load	11.12 Three-Phase Power	11.13 Power Measurement and the Two-Wattmeter Method
--	---	--	-------------------------------------	----------------------------	--

CHAPTER 12 Frequency Response, Filters, and Resonance

291

12.1 Frequency Response	12.2 High-Pass and Low-Pass Networks
12.3 Half-Power Frequencies	12.4 Generalized Two-Port, Two-Element Networks
12.5 The Frequency Response and Network Functions	12.6 Frequency Response from Pole-Zero Location
12.7 Ideal and Practical Filters	12.8 Passive and Active Filters
12.9 Bandpass Filters and Resonance	12.10 Natural Frequency and Damping Ratio
12.11 RLC Series Circuit; Series Resonance	12.12 Quality Factor
12.13 RLC Parallel Circuit; Parallel Resonance	12.14 Practical LC Parallel Circuit
12.15 Series-Parallel Conversions	12.16 Locus Diagrams
12.17 Bode Diagrams	12.18 Observations
12.19 Special Features of Bode Diagrams	12.20 Summary of First-Order Filters
12.21 Second-Order Filters	12.22 Butterworth Filters
12.23 Scaling the Frequency Response of Filters	

CHAPTER 13 Two-Port Networks

335

13.1 Terminals and Ports	13.2 Z-Parameters	13.3 T-Equivalent of Reciprocal Networks
13.4 Y-Parameters	13.5 Pi-Equivalent of Reciprocal Networks	13.6 Application of Terminal Characteristics
13.7 Conversion between Z- and Y-Parameters	13.8 h-Parameters	13.9 g-Parameters
13.10 Transmission Parameters	13.11 Interconnecting Two-Port Networks	
13.12 Choice of Parameter Type	13.13 Summary of Terminal Parameters and Conversion	

CHAPTER 14 Mutual Inductance and Transformers

359

14.1 Mutual Inductance	14.2 Coupling Coefficient	14.3 Analysis of Coupled Coils
14.4 Dot Rule	14.5 Energy in a Pair of Coupled Coils	
14.6 Conductively Coupled Equivalent Circuits	14.7 Linear Transformer	
14.8 Ideal Transformer	14.9 Autotransformer	14.10 Reflected Impedance

CHAPTER 15 Circuit Analysis Using Spice and PSpice

387

15.1 Spice and PSpice	15.2 Circuit Description	15.3 Dissecting a Spice Source File
15.4 Data Statements and DC Analysis	15.5 Control and Output Statements in DC Analysis	15.6 Thévenin Equivalent
15.7 Subcircuit	15.8 Op Amp Circuits	15.9 AC Steady State and Frequency Response
15.10 Mutual Inductance and Transformers	15.11 Modeling Devices with Varying Parameters	15.12 Time Response and Transient Analysis
15.13 Specifying Other Types of Sources	15.14 Summary	

CHAPTER 16 The Laplace Transform Method

425

16.1 Introduction	16.2 The Laplace Transform	16.3 Selected Laplace Transforms
16.4 Convergence of the Integral	16.5 Initial-Value and Final-Value Theorems	16.6 Partial-Fractions Expansions
16.7 Circuits in the s-Domain	16.8 The Network Function and Laplace Transforms	

CHAPTER 17 Fourier Method of Waveform Analysis	448										
17.1 Introduction	17.2 Trigonometric Fourier Series	17.3 Exponential Fourier Series	17.4 Waveform Symmetry	17.5 Line Spectrum	17.6 Waveform Synthesis	17.7 Effective Values and Power	17.8 Applications in Circuit Analysis	17.9 Fourier Transform of Nonperiodic Waveforms	17.10 Properties of the Fourier Transform	17.11 Continuous Spectrum	
APPENDIX A Complex Number System	481										
APPENDIX B Matrices and Determinants	484										
INDEX	491										

Index

- A**
ABC sequence, 268, 280–281, 284–285, 288
AC generator, 266, 279
AC power, 237–265
 apparent, 244–248
 average, 239–241, 242, 254, 263–265
 complex, 244–248, 263–265
 energy exchanged between inductor/capacitor, 242–244
 instantaneous, 237–238, 242, 255
 maximum power transfer, 251–252, 265
parallel-connected networks, 248–249
power factor improvement, 250–251
quadrature, 241
reactive, 241, 244–248, 261, 277–278
real, 239–241
in RLC, 241–242
sinusoidal steady state, 238–239
AC wattmeter, 277, 283
Active circuits, 159–161, 193–194
 first-order, 159–161
 higher-order, 193–194
Active elements, 7–8
Active filters, 299–300
Active phase shifter, 161
Admittance, 214, 223, 260–261, 328–329
 combination of, 215
 coupling, 219
 diagram, 216
 input, 219, 229
 in parallel, 215
 self-, 219
 in series, 215
 transfer, 219, 229
Admittance parameters, short-circuit (*see* Y-parameters)
Air-core transformers, 365
Ampere, 1–3
Ampere-hours, 5
Ampere-turn dot rule, 368
Ampere-turns, 368
Amplifiers, 72–116
 differential/difference, 83–84
 feedback in, 73–74
 integrator-summer, 87
 leaky integrator, 86
 model of, 72–73
 operational (*see* Op amps)
 saturation, 75–78
Analog computers, 88–89
Analog-to-digital converter, 93–94
Analysis methods, 37–71 (*See also* Laws, Theorems)
 branch current, 37, 49–50, 57–58
 determinant, 38–40
 Laplace transform, 425–447
 matrix/matrices, 38–40
 mesh (loop) current, 37–38, 44, 50, 58, 60, 64–65, 226, 234
 node voltage, 40–41, 52–53, 59, 61, 63, 64, 219, 227–228
Apparent power, 244–248
 in three-phase system, 277–278
Attenuator, 31
Autotransformers, 369, 380
Average power, 239–241, 242, 254, 263–265
- B**
Bandpass filters, 300–301
Bandwidth, 321–322
Batteries, 5
Bode diagram, 310
 special features of, 310–311
Branch current method, 37, 49–50, 57–58
- C**
Capacitance/capacitors, 6, 7, 9, 12, 33, 143–146, 173, 194–196, 232
DC steady state in, 152–153
discharge in a resistor, 143–144
distributed, 7
energy exchange between inductors and, 242–244
establishing DC voltage across, 145–146
lossy, 323–324
in parallel, 26–27, 31
in series, 25–26, 31
Capacitive reactance, 214
Capacitive susceptance, 214
CBA sequence, 268, 281–282, 288
Center frequency, 300
Centi, 2
Circuit analysis, 387–424
 applications of Fourier method in, 456–459
circuit description, 387–388
DC analysis, 388–392
Using Spice and PSpice, 387–424
- Circuits:
 analysis methods, 37–71
 concepts, 7–23
 diagrams of, 12–13
 differentiator, 88
 elements in parallel, 26–27
 elements in series, 25–26
 first-order, 143–178
 active, 159–161
 higher-order, 179–208
 active, 193–194
 integrator, 85–87
 inverting, 79
 laws regarding, 24–36
 locus diagram, 307–310
 noninverting, 80–82
 noninverting integrators, 207
 polyphase, 266–290
 RC (*see* RC circuits)
 RL (*see* RL circuits)
 RLC (*see* RLC circuits)
 series-parallel conversions, 306–307
 sign convention, 8–9
 sinusoidal (*see* Sinusoidal circuits):
 Sinusoidal steady-state circuits)
 summing, 79–80
 tank, 305, 309
 two-mesh, 185–186, 203
 voltage-current relations, 9
Close coupling, 361
Coils, 267–268, 277, 320
coupled, 362–363, 371
 energy in a pair of, 364
self-inductance of, 359
In series with a known resistance, 224
Column matrix, 484
Comparators, 92–93
Complex frequency, 186–187, 196–197, 203
forced response and, 190–191
frequency scaling, 192–193
generalized impedance in s-domain circuits, 187–188
magnitude scaling, 192–193
natural response and, 191–192
network function and, 188–190
pole-zero plots, 188–190
Complex frequency domain, 425
Complex inversion integral, 425

- Complex number system, 481–483
 conjugate of, 483
 difference of, 482
 division of, 483
 modulus or absolute value, 482
 multiplication of, 482–483
 plane, 481
 rectangular form, 481
 representations of, 481–482
 sum of, 482
 trigonometric form, 482
 vector operator, 481
- Complex power, 244–248, 263–265
- Computers:
 analog, 88–89
 circuit analysis using, 387–424
PSpice program (*see* Spice and *PSpice*)
Schematic Capture program, 387
Spice program (*see* Spice and *PSpice*)
- Conductance, 1, 214
- Conduction, 2
- Constant quantities, 4
- Convergence region of Laplace integral, 428
- Cosine wave, 119
- Coulomb, 1–3
- Coupled coils, 362–363
 energy in a pair of, 364
- Coupling admittance, 219
- Coupling coefficient, 361
- Coupling flux, 361
- Cramer's rule, 39, 488–489
- Critically damped, 179, 181–182, 185, 302
- Current, 1–2
 branch, 37, 49–50, 57–58, 223, 326
 constant, 4
 DC in inductor, 148
 division, 28–29
 in frequency domain, 216
 Kirchhoff's law, 25, 37, 40
 load, 270–271
 loop, 37–38
 magnetizing, 366
 mesh, 37–38, 44, 50, 58, 60, 64–65,
 216–219, 226, 234
 natural, 362
 Norton equivalent, 45–47, 236
 phase, 270–271
 phasor, 211–214, 458
 relation to voltage, 9
 variable, 4
- D**
- Damped sinusoids, 131
- Damping, 179–185
 critically damped, 179, 302
 RLC circuits in parallel, 185
 RLC circuits in series, 181–182
- Damping (*Cont.*)
 overdamped, 179, 302
 RLC circuits in parallel, 183–184
 RLC circuits in series, 180–181
 underdamped, 179, 302
 RLC circuits in parallel, 184–185
 RLC circuits in series, 182
- Damping ratio, 302
- DC analysis, 388–392
 output statements, 392–394
- DC current, establishing in an inductor, 148
- DC steady state in inductors/capacitors, 152–153
- DC voltage across capacitor, 145–146
- Delta system, 269
 balanced loads, 270–271
 equivalent wye connections and, 272–273
 unbalanced loads, 274
- Determinant method, 38–40
- Diagonal matrix, 484
- Differentiator circuit, 88
- Diode, 13, 22, 23
 forward-biased, 13
 ideal, 22, 23
 operating point, 23
 reverse-biased, 13
 terminal characteristic, 23
- Direct Laplace transform, 425
- Dirichlet condition, 449–450, 459
- Displacement neutral voltage, 275
- Dissipation factor, 323
- Dot rule, 363, 373–374, 399
 ampere-turn, 368
- Dynamic resistance, 13
- E**
- Effective (RMS) value, 123–124
- Eigenvalues, 489
- Eigenvectors, 489
- Electric charge, 2–3
- Electric current, 2–3
- Electric potential, 3
- Electric power, 4
- Electrical units, 1–4
- Electrons, 2–3, 5
- Elements:
 active, 7–8
 nonlinear, 36
 passive, 7–8
- Energy (*See also* Power)
 in a pair of coupled coils, 364
 exchange between inductors and capacitors, 242–244
 kinetic, 3
 potential, 3
 work, 2, 3
- Energy density, 461
- Euler's formula, 482
- Euler's identity, 213
- Exponential excitation, response to:
 RC circuits, 158
 RL circuits, 158
- Exponential function, 128–130, 148–150
- F**
- Faraday's law, 361, 365
- Farads, 2, 9, 389
- Feedback in amplifier circuits, 73–74
- Femto, 389
- Filters, 298–302, 311–313
 active, 299–300
 bandpass, 300–301
 high-pass, 160
 low-pass, 89–90, 297
 passive, 299–300
 scaling frequency response of, 313–314
- First-order circuits, 143–178
 active, 159–161
- Floating source, 83
- Flux:
 coupling, 361
 leakage, 361
 linking, 361
 mutual, 365
- Force, 1, 2
- Forced response, 145
 network function and, 190–191
- Fourier integral, 459
- Fourier method, 448–480
 analysis using computers, 407
 circuit analysis and, 456–459
 effective values and power, 455–456
 exponential series, 450–451,
 469–471, 477–479
 trigonometric series, 448–450,
 463–469, 474–475
 waveform symmetry, 451–454
- Fourier transform:
 inverse, 459–461
 of nonperiodic waveforms, 459–461
 properties of, 461–462
- Frequency, 1, 119
 center, 300
 complex, 186–187, 196–197, 203
 half-power, 296
 natural, 205, 302
 operating, 306
 scaling, 192–193
 scaling of response for filters, 313–314
- Frequency domain, 214
 voltage and current division in, 216
- Frequency response, 89, 291–292
 computer circuit analysis of, 397–398
 high-pass networks, 292–295
 low-pass networks, 292–295
 network function and, 297
 parallel resonance and, 304–305

- Frequency response (*Cont.*)
 from pole-zero location, 297–298
 scaling for filters, 313–314
 series resonance and, 302–303
 two-port/two-element networks,
 296
- Frequency scaling, 192–193
- G**
- Gain, open loop, 73
 Generators:
 AC, 266, 279
 three-phase, 267–268
 two-phase, 266–267
- Giga, 2, 389
- g-parameters, 342, 345–346
- H**
- Half-power frequency, 296
 Half-wave symmetry, 453, 463–464
 Harmonics, 134, 454–455, 456–459,
 471
 Heaviside expansion formula, 430,
 436–437
- Henry, 1, 9, 389
- Hermitian matrix, 485
- Hertz, 1
- Higher-order circuits, 179–208
 active, 193–194
- High-pass filter, 160
- High-pass networks, 292–295
- Homogeneous solution, 143, 145
- Horsepower, 5
- h-parameters, 341–342, 345–346,
 353–354
- hybrid parameters, 341–342, 345–346,
 353–354
- I**
- Ideal transformers, 367–368
 Impedance, 198, 214–216, 222–223,
 232, 287–290
 combinations of, 215
 diagram, 215
 input, 218, 228
 in parallel, 215
 reflected, 369–371
 in s-domain, 187–188
 in series, 215
 sinusoidal steady-state circuits,
 214–216
 transfer, 218, 228
- Impedance parameters, open-circuit
 (*see* Z-parameters)
- Impulse function:
 sifting property, 128
 strength, 127
 unit, 126–128
- Impulse response:
 RC circuits and, 156–157
 RL circuits and, 156–157
- Inductance/inductors, 1, 7–9, 11,
 15, 20
 DC steady state in, 152–153
 distributed, 7
 energy exchange between capacitors
 and, 242–244
 establishing DC current in, 148
 leakage, 365
 mutual, 359
 in parallel, 26–27, 30–31
 self-, 359
 in series, 25–26
- Induction motors, 262, 264
- Inductive reactance, 214
- Inductive susceptance, 214
- Input admittance, 219, 229
- Input impedance, 218, 228
- Input resistance, 43, 59
- Instantaneous power, 237–238, 242,
 255, 266–267
- Integrator circuit, 85–87
 initial conditions of, 87
 leaky, 86
 noninverting, 207
- International System of Units (SI), 1
- Inverse Fourier transform, 459–461
- Inverse hybrid parameters, 342, 345
- Inverse Laplace transform, 425
- Inversion integral, complex, 425
- Inverting circuit, 79
- Ions, 2
- Iron-core transformer, 365
- J**
- Joule, 1–4
- K**
- Kelvin temperature, 1
- Kilo, 1, 389
- Kilowatt-hour, 5
- Kinetic energy, 3
- Kirchhoff's current law (KCL), 25,
 37, 40
- Kirchhoff's voltage law (KVL), 24,
 38, 427
- L**
- Lag network, 208
- Laplace transform method, 425–447
 circuits in s-domain, 431–432
 convergence of the integral, 428
 direct, 425
 final-value theorem, 428–429
 Heaviside expansion formula, 430,
 436–437
 initial-value theorem, 428–429
 inverse, 425
 network function and, 432–433
 partial-fraction expansion, 429–430
 selected transforms, 427
- Laplace's expansion theorem, 488
- Laws, 24–36 (*See also* Theorems)
 Kirchhoff's current, 25, 37, 40
 Kirchhoff's voltage, 24, 38, 427
 Lenz's, 363
 Ohm's, 9, 47
 LC circuits, parallel, 305–306
 Lead network, 207–208
 Leakage flux, 361
 Leakage inductance, 365
 Length, 1
 Lenz's law, 363
 Lightning, 22
 Line spectrum, 454–455
 Linear transformers, 365–367, 378–379
 Linking flux, 361
 Load current, 270–271
 Locus diagram, 307–310
 Loop current method (*see* Mesh current
 method)
 Loop currents, 37–38
 Lossy capacitors, 323–324
 Low-pass filters, 89–90, 297
 Low-pass networks 292–295
- M**
- Magnetic flux, 1
 Magnetic flux density, 1
 Magnetic flux linkage, 361
 Magnetizing current, 366
 Magnitude scaling, 192–193, 201–202
 Mass, 1
 Matrix (matrices), 484–490
 adding, 485–486
 characteristic, 484
 column, 484
 diagonal, 484
 eigenvalues of square, 489
 eigenvectors of square, 489
 Hermitian, 485
 inversion by determinants, 488–489
 multiplication by a scalar, 487
 multiplying, 486–487
 nonsingular, 485–486
 null, 484
 row, 484
 simultaneous equations, 484
 square, 484, 487–490
 subtracting, 485
 symmetric, 485
 types of, 484–485
 unit, 484
 Z-matrix, 217
- Matrix method, 38–40, 51–52
- Maximum power transfer, 251–252, 265
- Maximum power transfer theorem,
 47–48
- Mega, 2, 389
- Mesh current/mesh current method,
 37–38, 44, 50, 58, 60, 64–65, 226,
 234
- sinusoidal circuits and, 216–219

- Meter, 1
 Methods, analysis (*see Analysis methods*)
 Micro, 2, 389
 Milli, 2, 389
 Minimum power, 35
 Motors, induction, 262, 264
 Mutual flux, 365
 Mutual inductance, 359
 computer circuit analysis of, 398–400
 conductively coupled equivalent circuits and, 364–365
 coupled coils and, 262–263
 coupling coefficient and, 361
 dot-rule and, 363
- N**
 Nano, 2, 389
 Natural current, 362
 Natural frequency, 205, 302
 Natural response, 145
 network function and, 191–192
 Network function, 188–190
 complex frequency and, 188–190
 forced response, 190–191
 frequency response and, 297
 Laplace transform and, 432–433
 natural response, 191–192
 pole-zero plots, 188–190
 Network reduction, 41–43
 Network(s):
 conversion between Z- and Y-parameters, 340–341
 g-parameters, 342, 345–346
 high-pass, 292–295
 h-parameters, 341–342, 345–346, 353–354
 lag, 208
 lead, 207–208
 low-pass, 292–295
 nonreciprocal, 336
 parallel-connected, 248–249
 parameter type, 345
 passive in the s-domain, 189–190
 pi-equivalent, 339
 reciprocal, 336, 337, 339
 T-equivalent, 337
 terminal characteristics, application of, 335, 339–340
 terminal parameters and conversion, 345–346
 T-parameters, 343–346
 two-mesh, 446
 two-port, 335–358
 two-port/two-element, 296
 Y-parameters, 337–339, 344–345, 349
 Z-parameters, 335–337, 343–345, 346–348, 350–351
 Newton, 1, 2
 Newton-meter, 2
- Node:
 principal, 25
 simple, 25
 Node voltage method, 40–41, 52–53, 59, 61, 63, 64, 219, 227–228
 sinusoidal circuits and, 219
 Noninverting circuits, 81–82
 Noninverting integrators, 207
 Nonlinear element, 36
 Nonlinear resistors, 13–14
 dynamic resistance, 13
 static resistance, 13
 Nonperiodic functions, 125
 Nonreciprocal networks, 336
 Nonsingular matrix, 485
 Norton equivalent current, 45–47, 236
 Norton's theorem, 45–47, 62, 220, 230–231, 235–236
 sinusoidal circuits and, 220
 Null matrix, 484
 Number system, complex (*see Complex number system*)
- O**
 Ohm, 1, 9, 389
 Ohm's law, 9, 47
 Op amps, 75–78
 circuit analysis of, 78–79
 circuits containing several, 84–85
 computer circuit analysis of, 397
 saturation, 75–78
 voltage follower, 82, 109–110
 Open-loop gain, 73
 Operating point, diode, 13–14, 23
 Operational amplifiers (*see Op amps*)
 Output resistance, 43
 Overdamping, 179, 302
 parallel RLC circuit, 183–184
 series RLC circuit, 180–181
- P**
 Parallel analog-to-digital converter, 93–94
 Partial-fraction expansion, 429–430
 Particular solution, 143, 145
 Passive elements, 7–8
 Passive filters, 299–300
 Passive network in the s-domain, 189–190
 Passive phase shifter, 161
 Periodic functions, 117–118, 237–238, 448
 average/effective (RMS) values, 123–124
 combination of, 122
 Periodic pulse, 117–118
 Periodic tone burst, 118
 Phase angle, 1, 196–197, 210–213
 Phase current, 270–271
 Phase shift, 119–122
 Phase shifter, 161
 active, 161
 passive, 161
- Phasor voltage, 269–270
 Phasors, 211–214
 defining, 211–212
 diagrams, 212
 equivalent notations of, 213
 phase difference of, 211
 voltage, 225
 Pico, 2, 389
 Pi-equivalent network, 339
 Plane angle, 1
 Polarity, 8–9, 29, 267–268
 instantaneous, of coil terminals, 363
 Pole zero plots (*see Zero pole plots*)
 Polyphase circuits, 266–290
 ABC sequence, 268, 280–281, 284–285, 288
 CBA or ABC, 290
 CBA sequence, 268, 281–282, 288
 delta system, 269
 balanced loads, 270–271
 equivalent wye connections and, 272–273
 unbalanced loads, 274
 instantaneous power, 266
 phasor voltages, 269–270
 power measurement with wattmeters, 277–278
 single-line equivalent circuit for balanced three-phase loads, 273
 three-phase power and power factor, 276–277
 three-phase systems, 267–268
 two-phase systems, 266–267
 wye system, 269
 balanced loads, 271–272
 equivalent delta connections and, 272–273
 unbalanced four-wire loads, 274–275
 unbalanced three-wire loads, 275–276
- Potential energy, 3
 Potentiometer, 31
 Power, 1–2, 18–19, 21, 95 (*See also Energy*)
 absorbed, 95
 AC, 237–265
 apparent, 244–248
 average, 239–241, 242, 254, 263–265
 complex, 244–248, 263–265
 effective values and, 455–456
 electrical, 4
 instantaneous, 237–238, 242, 255, 266–267
 minimum, 35
 quadrature, 241
 reactive, 241, 244–248, 261, 277–278
 real, 239–241
 in sinusoidal steady state, 238–239
 superposition of average, 252–253
 three-phase, 276–277
 in three-phase systems, 276–277
 transfer theorem, maximum, 47–48

- Power factor, 240, 256–259
improvement, 250–251
in three-phase systems, 276–277
- Power transfer, maximum, 251–252
- Power triangle, 244–248, 258–260
- Primary winding, 365
- Principal node, 25
- PSpice (*see* Spice and PSpice)
- Pulse, response of first-order circuits to, 155–156
- Q**
- Quadrature power, 241
- Quality factor, 304
in RLC series circuit, 319
- R**
- Radian, 1
- Random signals, 131–132
- RC circuit:
complex first-order, 150–151
impulse response of, 156–157
in parallel, 138, 144, 157
Y- and Z-loci for, 308
response to exponential excitations, 158
response to pulse, 155–156
response to sinusoidal excitations, 159
in series, 145–146, 155–157,
172–174, 222, 232
source-free, 143–144
step response of, 157
- Reactance:
capacitive, 214
inductive, 214
- Reactive power, 241, 244–248, 261
in three-phase systems, 277–278
- Real power, 239–241
- Reciprocal networks, 336
pi-equivalent of, 339
- Reflected impedance, 369–371
- Resistance/resistors, 9, 10
capacitor discharge in, 143–144
distributed, 7
dynamic, 13
input, 43, 59
nonlinear, 13–14
output, 43
in parallel, 26–27, 28–29
in series, 25–26, 28
static, 13
transfer, 44, 60
- Resonance, 300–301, 316, 322, 327–329
parallel, 304–305
series, 302–303
- RL circuits:
complex first-order, 150–151
impulse response of, 156–157
in parallel, 157
Y-locus for, 309
response to exponential excitations, 158
- RL circuits (*Cont.*)
response to pulse, 155–156
response to sinusoidal excitations, 159
in series, 148, 157–158, 170, 173
source-free, 146–147
step response of, 157
two-branch, 326
- RLC circuits:
AC power in, 241–242
in parallel, 183–185, 195–196
critically damped, 185
overdamped, 183–184
underdamped, 184–185
quality factor, 319
resonance:
parallel, 304–305
series, 302–303
in series, 179–182, 194–195
critically damped, 181–182
natural resonant frequency, 203
overdamped, 181–182
scaled element values, 206
s-domain impedance, 188
transient current, 202
transient voltage, 203
underdamped, 182
Y-locus of, 308–309
- Root-mean-square (RMS), 123–124
average/effective values, 123–124
- Row matrix, 484
- S**
- Saturation, of operational amplifiers, 75–78
- Sawtooth wave, 448, 450, 454–455, 474
- Scaling:
frequency, 192–193
frequency response of filters, 313–314
magnitude, 192–193, 201–202
- s-domain circuits, 187–194, 203, 431–432
impedance, 187–188
impedance of series RLC circuit, 188
passive network in, 189–190
- Second, 1
- Secondary winding, 365
- Self-admittance, 219
- Self-inductance, 359
- Sensitivity, 109–110
analysis using computers, 407
- SI units, 1
- Siemens, 1
- Signals:
nonperiodic, 125
periodic, 117–118, 237–238, 448
random, 131–132
- Simple node, 25
- Sine wave, 117, 119
- Sinusoidal circuits:
Norton's theorem and, 220
steady-state node voltage method
and, 219
- Thevenin's theorem and, 220
- Sinusoidal excitation, response in:
RC circuits, 159
RL circuits, 159
- Sinusoidal functions, 119
- Sinusoidal steady-state circuits, 209–236
admittance, 214–216
element responses, 209–211
impedance, 214–216
mesh current method and, 216–219
phase angle, 210–213
phasors, 211–214
voltage/current division in frequency
domain, 216
- Software (*see* Computers; Spice and
PSpice)
- Spice and PSpice, 387–424
AC steady state, 397–398
.AC statement, 398
independent sources, 397–398
.PLOT AC statement, 398
.PRINT AC statement, 398
- data statements:
controlled sources, 391
current-controlled sources, 391
dependent sources, 390–392
independent sources, 389–390
linearly dependent sources, 390
passive elements, 388–389
scale factors and symbols, 389
voltage-controlled sources, 391
- DC analysis:
output statements, 392–394
using, 388–392
- exponential source, 402–403
- Fourier analysis, 407
- frequency response, 397–398
- modeling devices, 401–402
- mutual inductance, 398–400
- op amp circuit analysis, 397
- pulse source, 403
- sensitivity analysis, 407
- sinusoidal source, 405
- source file:
control statements, 388
data statements, 388
dissecting, 388
.END statement, 388
output statements, 388
title statement, 388
- specifying other sources, 402–406
- SUBCKT statement, 395
- Thevenin equivalent, 394–395
.TF statement, 394
- time response, 402
- transformers, 398–400
- transient analysis, 402
- s-plane plot, 204
- Square matrix, 484, 487–490
- Static resistance, 13
- Steady state, 143
- DC in inductors/capacitors, 152–153

- Step function, unit, 125–126
 Steradian, 1
 Summing circuit, 79–80
 Superposition, 44–45, 61, 63–65, 111
 of average powers, 252–253
 Susceptance:
 capacitive, 214
 inductive, 214
 Switching, 143
 transition at, 153–154
 Symmetric matrix, 485
 Symmetry:
 half-wave, 453, 463–464
 waveforms, 451–454, 464
 Synthesis, waveform, 455, 474
- T**
 Tank circuit, 305, 309
 Temperature, Kelvin, 1
 T-equivalent network, 337
 Tera, 2, 389
 Terminal characteristics, application of, 335, 339–340
 Terminal parameters and conversion, 345–346
 Tesla, 1
 Theorems (*See also Laws*):
 final-value, 428–429
 initial-value, 428–429
 Laplace's expansion, 488
 maximum power transfer, 47–48
 Norton's, 45–47, 62, 220, 230–231, 235–236
 Thevenin's, 45–47, 55–56, 62–63, 220, 230–231, 235–236, 394–395
 Thevenin equivalent voltage, 45
 Thevenin's theorem, 45–47, 55–56, 62–63, 220, 230–231, 235–236, 394–395
 sinusoidal circuits and, 220
 Three-phase systems (*see Polyphase circuits*)
 Time, 1
 Time constant, 129, 148–150
 Time domain, 214
 vs. s-domain, 425
 Time function, 4, 117–142
 nonperiodic, 117, 125
 periodic, 117–118, 122
 random, 117
 Time response, computer circuit analysis of, 402
 Time shift, 119–122
 Tone burst, repeatedly in radar signal, 137
 T-parameter, 341–346
 Transducer, 104
 Transfer admittance, 219, 229
- Transfer function, 188–190, 204, 320–321
 command using Spice/PSpice, 394
 Transfer impedance, 218, 228
 Transfer resistance, 44, 60
 Transformers, 264, 359–386
 air-core, 365
 auto-, 369, 380
 computer circuit analysis of, 398–400
 ideal, 367–368
 iron-core, 365
 linear, 365–367, 378–379
 rating, 260–261
 reflected impedance of, 369–371
 Transients, 143
 computer circuit analysis of, 402
 Two-mesh circuits, 185–186, 203
 Two-mesh networks, 446
 Two-port networks, 296, 335–358
 cascade connection, 344–345
 converting between Z- and Y-parameters, 340–341
 g-parameters, 342, 345–346
 h-parameters, 341–342, 345–346, 353–354
 interconnecting, 343–345
 parallel connection, 344
 series connection, 343–344
 T-equivalent of, 337
 terminals and, 335
 T-parameters, 343, 345–346
 in a cascade combination, 344
 Y-parameters, 337–339, 344–345, 349
 Z-parameters, 335–337, 343–345, 346–348, 350–351
- U**
 Underdamping, 179, 182, 184–185, 302
 Unit delta function, 126–128
 Unit impulse function, 126–128
 Unit impulse response, 157
 Unit matrix, 484
 Unit step function, 125–126
 Unit step response, 157
- V**
 Vector operator, 481
 Volt, 1, 3
 Voltage, 3, 18
 DC voltage across capacitor, 145–146
 displacement neutral, 275
 Kirchhoff's law, 24, 38, 427
 node, 40–41, 52–53, 59, 61, 63, 64, 219, 227–228
 phasor, 269–270
 polarities for three-phase systems, 267–268
 relation to current, 9
 sign conventions for, 8–9
- Y**
 Y-parameters, 337–339, 344–345, 349
 converting between Z-parameters and, 340–341
- Z**
 Zero pole plots, 188–191, 200, 204–205
 frequency response from, 297–298
 Z-matrix, 217
 Z-parameters, 335–337, 343–345, 346–348, 350–351
 converting between Y-parameters and, 340–341

