




# ELECTRONIC DEVICES AND CIRCUITS

Ref  
621.3815  
E138  
2014



R4  
Cal. 3215  
E138  
2014  
4

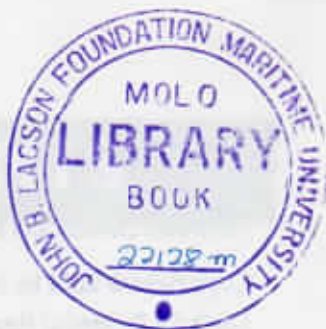

# ELECTRONIC DEVICES AND CIRCUITS



3G eLEARNING

# TABLE OF CONTENTS

<b>1. Introduction Electronics Devices</b>	<b>4.1 Simple Switching Network</b> .....	<b>107</b>
1.1 Bridges .....	4.1.1 Circuit Switching Networks .....	109
1.2 Potentiometers .....	<b>4.2 Circuit Switching Concepts</b> .....	<b>109</b>
1.3 A.C & D.C Current Probes .....	4.2.1 Space Division Switching .....	110
1.4 Extension Of Instrument Ranges .....	4.2.2 Time Division Multiplexing .....	113
1.5 Q Meter .....	<b>4.3 Control Signalling</b> .....	<b>115</b>
1.6 Waveform Analyzer .....	4.3.1 Channel and Common Channel Signalling .....	116
1.7 Digital Voltmeter .....	<b>4.4 Brief Idea of SS7</b> .....	<b>118</b>
1.8 Digital Multimeter .....	4.4.1 Advantages of SS7 .....	119
1.9 Shielding And Grounding .....	<b>4.5 Packet Switching</b> .....	<b>120</b>
<b>2. Electronics Measurements</b>	4.5.1 Packet-Switching Principles .....	123
2.1 Resistance (R) Measurement .....	<b>4.6 Routing in Switching Networks</b> .....	<b>124</b>
2.2 Self-Inductance (L) Measurement .....	4.6.1 Routing in Circuit Switching Network .....	124
2.3 Capacitance (C) Measurement .....	4.6.2 Routing in Packet Switching Networks .....	125
2.4 Voltage And Current Measurement .....	<b>4.7 X.25 in Computer Networking</b> .....	<b>126</b>
2.5 Power Measurement .....	4.7.1 X.25 Applications .....	127
2.6 Power Factor Measurement .....	<b>5. Combinational Circuits Objectives</b>	
2.7 Energy Measurement .....	<b>5.1 Adder</b> .....	<b>129</b>
2.7.1 Time, Phase and Frequency Measurements .....	5.1.1 Half Adder .....	129
2.7.2 Measurement of Phase .....	5.1.2 Full-adder .....	130
2.7.3 Frequency Measurements .....	<b>5.2 Subtractor</b> .....	<b>131</b>
<b>3. Circuits Analysis</b>	5.2.1 Half-subtractor .....	132
3.1 Circuits .....	5.2.2 Full subtractor .....	133
3.1.1 Active And Passive Element .....	<b>5.3 Encoder</b> .....	<b>134</b>
3.2 Kirchhoff's Law .....	5.3.1 Binary Encoders .....	134
3.3 Mesh and Nodal Analysis .....	5.3.2 Priority Encoders .....	135
<b>4. Circuit Switching</b>	<b>5.4 Decoder</b> .....	<b>137</b>

<b>6. Combinational Logic Circuit Implementation</b>	<b>8. Three Phase Circuits</b>
6.1 Multiplexers .....142	8.1 Neutral Currents in Three Phase Wye Systems.....189
6.1.1 Synthesis of Logic Functions Using Multiplexers .....146	8.1.1 Wye and Delta Configurations ..191
6.1.2 Multiplexer Synthesis Using Shannon's Expansion .....149	8.1.2 Voltage, Current, and Power Measurements in a Wye-Connected Circuit.....191
6.2 Demultiplexer.....151	8.1.3 Voltage, Current, and Power Measurements in a Delta-Connected Circuit .....192
6.3 Code-converters .....154	8.2 Measurement of Three-phase Power... 195
6.4 Comparators.....155	8.2.1 The Two-Wattmeter Method ....196
<b>7. Standard Integrated Circuits (ICs)</b>	8.2.2 Neutral Current in an Unbalanced Three-phase Load.....197
7.1 Resistor-Transistor Logic (RTL) .....158	8.2.3 Advantages of Three-phase Systems.....197
7.2 Diode-Transistor Logic (DTL).....161	8.3 The Fundamentals of Three-Phase Power Measurements.....198
7.3 Transistor-Transistor Logic (TTL)..163	8.3.1 Three-Phase Systems.....198
7.3.1 Test Parameters for TTL Devices... 166	8.4 Delta Connection .....201
7.4 Emitter-Coupled Logic (ECL).....167	8.4.1 Wye and Delta Comparison.....202
7.4.1 Implementation.....169	8.4.2 Power Measurements .....203
7.4.2 Operation.....170	8.4.3 Configuring Measurement Equipment.....205
7.5 Integrated Circuit (IC).....171	8.5 Power System Fault Analysis ..... 206
7.5.1 Design.....171	8.5.1 Derivation of Sequence Networks . 208
7.5.2 The Manufacturing Process .....171	8.6 Voltage Unbalance on the Performance of Three-Phase Induction Motor ....210
7.6 High Threshold Logic (HTL) .....174	8.6.1 Voltage Variations and Unbalance .. 211
7.6.1 Advantages.....175	8.7 Three-Phase Induction Motor Model... 212
7.6.2 Disadvantages.....175	8.8 Assessment of Voltage Unbalance ..213
7.7 NMOS and CMOS Logic Gates .....176	
7.7.1 Overview of CMOS.....178	
7.7.2 Important Feature of CMOS ....178	
7.7.3 Test parameters of CMOS.....179	
7.7.4 Important Feature of NMOS....183	
7.7.5 CMOS versus TTL.....183	

## Bibliography