



Fundamentals of TTI a=TaITS

3G E-LEARNIJ.G

FUNDAMENTALS OF ELECTRICAL CIRCUITS

A
3G E-LEARNING

- AMENIALS OF ELECTRICAL CIRCUITS

F-LEARNING

2020 3G E-learning LLC

Church Street

1 #3514

ew York, NY 10008

of America

info@3ge-learning.com

Authored and Edited by 3G E-learning LLC, USA

ISBN: 978-1-98463-843-4

This book contains information obtained from highly regarded resources. A Wide variety of references are listed. Reasonable efforts have been made to publish reliable data and information, but the authors, editors, and the publisher cannot assume responsibility for the legality of all materials or the consequences of their use. The authors, editors, and the publisher have attempted to trace the copyright holders of all material in this publication and express regret to copyright holders if permission to publish has not been obtained. If any copyright material has not been acknowledged, let us know so we may rectify in any future reprint. Registered trademark of products or corporate names are used only for explanation and identification without intent to infringe.

Notice: Registered trademark of products or corporate names are used only for explanation and identification without intent of infringement. Case Studies and/or Images presented in the book are the proprietary information of the respective organizations, and have been used here specifically and only for educational purposes. Although care has been taken to check accuracy of formulas and procedures, the detailed methods should be tested further on a small scale before being adopted commercially.

For more information about 3G E-Learning LLC and its products, visit www.3ge-learning.com

TABLE OF CONTENTS

Preface

xiii

Chapter 1 Circuit Topologies and DC Excitation 1

Introduction	1
Introductory Concepts	2
Conductors, Insulators, and Electron Flow	2
Electric Circuits	6
Voltage and Current	8
Voltage and Current in a Practical Circuit	20
Conventional Versus Electron Flow	22
Electrical Properties of a Material	25
Resistivity	25
Conductivity	26
Dielectric Strength	27
Temperature Coefficient of Resistance	27
Thermoelectricity	28
Passive Elements	28
Resistors	29
Capacitors	29
Coils	31
Filter Circuits (HPFs and LPFs)	31
Transformers	32
Network Laws and Theorems	32
Ohm's Law	33
Coulomb's Law	33
DC Circuit Rules	34
Kirchhoff's Circuit Laws	36
Voltage Divider	38
Theorems	40
Super Position Theorem	40
Thevenin's Theorem	41
Norton's Theorem	41

Maximum Power Transfer Theorem	42
Reciprocity Theorem	43
Compensation Theorem	43
Millman's Theorem	44
Tellegen's theorem	44
Substitution Theorem	44
Miller's Theorem	44
Summary	49
Multiple Choice Questions	50
Review Questions	51
References	52

Chapter 2 Transient Response **53**

Introduction	53
RC Circuits	54
RC Charging Circuit	55
RC Charging Circuit Curves	56
RC Time Constant, Tau	57
Source-Free RC Circuit	59
RC Series Circuit	64
RLCIRCUIT	67
RL Circuit Transient: Inductor Charging and Discharging	69
RL Series Circuit	72
Phase Angle	74
RLC Circuit	76
Applications:	77
RLC Series Circuit	78
Summary	85
Multiple Choice Questions	86
Review Questions	87
References	88

Chapter 3 AC Response and Polyphase Circuit **89**

Introduction	89
Reactance and Impedance	90
Types of Reactance	91
Impedance	92
How to Calculate Impedance	93
Single Phase AC Circuits	97

Generation of sinusoidal AC voltage	98
AC Power Analysis	100
Instantaneous and Average Power	100
Sinusoidal Steady-State Analysis	102
Sinusoidal Sources	103
Phaser Analysis	105
Three- Phase Circuits	108
Types of Connections in Three-Phase System	110
Transformer	111
Types of Transformers	112
Single Phase Voltage Transformer	114
Transformer Construction (single-phase)	114
Transformer Action	117
Electrical Power in a Transformer	120
Transformer Basics – Efficiency	120
Main Characteristics of a Transformer	122
Uses of Electrical Transformer	123
Tips for Troubleshooting an Electrical Transformer	123
Summary	128
Multiple Choice Questions	129
Review Questions	130
References	131

Chapter 4 Operational Amplifiers **133**

Introduction	133
Operational Amplifiers	134
Ideal OP AMP	139
The Noninverting Op Amp	140
The Inverting Op Amp	142
The Differential Amplifier	143
Summary	152
Multiple Choice Questions	153
Review Questions	155
References	156

Chapter 5 Capacitors and Inductors **159**

Introduction	159
Capacitors	160
Series and Parallel Capacitors	166
Inductors	169
Series and Parallel Inductors	174
Applications of Circuit	177

Integrator	177
Differentiator	179
Analog Computer	181
Summary	188
Multiple Choice Questions	189
Review Questions	191
References	192

Chapter 6 Magnetic Circuits **193**

Introduction	193
Magnetic circuits	194
Magnetic Circuit Analysis	196
Magnetic Material	200
Laws Governing Magnetic Circuits	202
Flux Linkage, Inductance and Energy	204
Inductance and Energy	204
Statically and Dynamically induced EMF	208
Torque	210
Properties of Magnetic Materials	211
Iron or Core Losses	212
A.C. Excitation	215
Permanent Magnets	215
Fundamentals	216
Experimental Techniques	221
Magnetic Materials for Permanent Magnets	226
Summary	234
Multiple Choice Questions	235
Review Questions	236
References	237

Chapter 7 Electrical Distribution System **239**

Introduction	239
Electrical Power Distribution System	240
Radial Electrical Power Distribution System	241
Ring Main Electrical Power Distribution System	242
Distribution System Planning	243
Basic Design Criteria	243
Network Configuration	246

Reliability Considerations	248
Electrical Power Transmission System	250
Factor to be considered for constructing a Generating Station	250
Transmission of Electrical Energy	251
Performance of Transmission Line	252
Power System Stability	253
Ferranti Effect in Power System	255
Corona Effect in Power System	257
Corona Effect in Transmission Line	257
Atmospheric Conditions for Corona in Transmission Lines	258
Electrical Insulator	259
Insulating Material	259
Porcelain Insulator	260
Glass Insulator	261
Polymer Insulator	262
Electrical Isolator Or Electrical Isolation Switch	263
Constructional Features of Double Break Isolators	264
Constructional features of Single Break Isolators	265
Design of Transmission Tower	267
Types of Transmission Tower	268
Summary	273
Multiple Choice Questions	274
Review Questions	276
References	277
 Index	 279

INDEX

A

AC Analysis 89,128
AC electrical transmission system 251
Air gap 193, 197, 199
Algebraic manipulation yields 141
Alternating current (AC) 23, 30
Amplifier circuit 143, 152
Analog computer 159, 182
Angular frequency 96, 97, 100

C

Capacitive reactance 30, 91
Capacitor current 91, 95, 96, 163
Capacitor voltage 58, 62, 63
Charging Current 56
Chemical identity 2
Chemical reaction 12
Circuit diagram 135
Communication systems 77
Complex Feedback Network 145
Conductivity 2, 25, 26, 27, 50
Conventional symbol 5
Cross-sectional area 170
Crystal structure 220, 229, 231
Current flow 194, 235
Customer substation 240, 243, 244, 245, 246,

D

DC electrical transmission system 251
DC voltage 54
Digital multimeter (DMM) 148
Direct current (DC) 30
Distribution Automation 248
Distribution networking 244
Distribution substation 240
Distribution system 239
Distribution Transformer 240
Dual in-line package (DIP) 135
Dynamic stability 254, 255

E

Electrical conductivity 3
Electrical continuity 5
Electrical current 28
Electrical energy 54
Electrical noise 180
Electrical power distribution system 240, 241, 242,243
Electrical resistance 256
Electrical transmission system 250
Electric circuit 2, 25, 49
Electric conductivity 2
Electric current 2, 4, 5, 6, 8, 15, 17, 23, 25, 26, 47, 49, 169, 189, 232, 233

Electric motor 2

Electron 2, 3, 4, 5, 6, 7, 8, 9, 11, 12, 13, 14, 15, 16, 17, 18, 19, 20, 22, 23, 25

Electronic circuit 1, 45, 49

Electron mobility 2, 11

Energy-storage elements 177

Equivalent capacitance 162, 167, 168, 169, 188

Equivalent circuit 63

Equivalent resistance 59, 62, 63

F

Ferranti effect 255, 256, 257

Filtering circuits 78

Flux linkage 193, 197, 204

H

High-pass filter (HPF) 31

Hypothetical electron 5, 7

I

Ideal inductor 173

Impedance 65, 74, 75, 80, 89, 92, 93, 94, 95, 96, 105, 106, 107, 115, 128, 129

Impedance dropping voltage 140

Impulse response 53

Inductance 31

Inductive reactance 91

Inductor 159, 169, 170, 171, 172, 173, 174, 175, 176, 188

Initial energy 60

Instantaneous value 67

Integrated-circuit (IC) 177, 188

Integrator 177

Inverting terminal 135, 136, 152

K

Kirchhoff's current law (KCL) 35, 37

Kirchhoff's rules 6

Kirchhoff's voltage law (KVL) 55

L

Low voltage (LV) 240

M

Magnetic circuit 193, 194, 196, 197, 199, 202, 203, 234, 235, 236

Magnetic core 195, 202, 203, 204

Magnetic field 193, 194, 201, 202, 203, 205, 207, 209, 212, 214, 216, 217, 218, 219, 220, 223

Magnetic flux 193, 194, 195, 199, 202, 203, 205, 206, 207, 234

Magnetic property 201

Maximum Current Rating 246

N

Natural response 60, 61

Network arrangement 243, 245, 248

Neutral conductor 109, 110

Nonideal op amp 134

Noninverting terminal 135, 136

Nonlinear capacitor 163

O

Open-loop voltage 136, 137

Operational flexibility 246

Oscillator circuit 76

Overcurrent and earth fault (OC/EF) 246

Overhead line insulator 260

Overhead Line (OHL) 243, 246, 273

P

Permittivity 25, 35

Phase angle 65, 74, 80, 81

Physical dimension 169, 188

Polyphase System 89, 90, 128

Positive charge 8

Potential energy 11, 12, 20, 22

Power dissipation 92, 104

Power system 248, 253, 254, 255, 256, 257, 258, 259, 263, 273, 276

Prevent saturation 179

Primary distribution feeder 240

R

Radio wave transmitters 77
 RC charging circuit 55, 57, 58
 RC circuit 53, 54, 55, 59, 60, 63, 67, 80, 85, 87
 RC Series circuit 64, 65
 Reactance 89, 90, 91, 92, 128
 Resistance 17, 25, 27, 28, 33, 49
 Resistive load 68, 71
 Resistivity 25, 26, 50
 Resistor value 145
 Resonant frequency signal 76
 Resonant LC circuit 78
 RF amplifiers 78
 RLC circuit 53, 76, 77, 81, 85, 86
 RL Circuit 67, 85
 RL Series Circuit 72, 73, 74, 75

S

Shift phase 162
 Signal Processing 77
 Single alternating voltage 90
 Single phase system 90 109
 Sinusoidal voltage 64
 Sinusoidal waveforms 102, 103
 Static electricity 4, 8, 11

Steady state stability 254
 Steady-state voltages 103
 Stray capacitance 142
 Supply interruption 246, 250
 Supply restoration 244, 245, 248, 249

T

Temperature coefficient 25, 28
 Thermoelectricity 25, 28, 50
 Threshold value 258
 Time response 54
 Topology 1, 49
 Transient fault 247
 Transient response 53, 85
 Transient stability 254, 255, 273
 Transmission line 244, 252, 253, 255, 256, 257, 258, 259, 265, 266, 268, 273, 276
 Tuning circuits 160

V

Uniform magnetic field 98, 99

V

Virtual ground 142
 Voltage/Current magnification 77