

10th Edition

ELECTRICITY

for Refrigeration, Heating and Air Conditioning



Russell E. Smith

CONTENTS

	Preface	vii
1	Electrical Safety Objectives 1 Key Terms 1 Introduction 2 1.1 Electrical Injuries 3 1.2 Dealing with Shock Victims 8 1.3 National Electrical Code® 8 1.4 Electrical Grounding 9 1.5 Circuit Protection 13 1.6 Circuit Lockout Procedures 14 1.7 Electrical Safety Guidelines 16 Summary 17 Review Questions 18	1
2	Basic Electricity Objectives 20 Key Terms 20 Introduction 21 2.1 Atomic Theory 21 2.2 Positive and Negative Charges 23 2.3 Flow of Electrons 24 2.4 Conductors and Insulators 27 2.5 Electric Potential 27 2.6 Current Flow 29 2.7 Resistance 30 2.8 Electric Power and Energy 31 2.9 Ohm's Law 33 2.10 Calculating Electric Power 36 Summary 36 Review Questions 38	20
3	Electric Circuits Objectives 40 Key Terms 40 Introduction 41 3.1 Basic Concepts of Electric Circuits 41 3.2 Series Circuits 43 3.3 Parallel Circuits 47 3.4 Series-Parallel Circuits 51 Summary 53 Review Questions 54	40
4	Electric Meters Objectives 56 Key Terms 56 Introduction 57 4.1 Electric Meters 58 4.2 Ammeters 64 4.3 Voltmeters 67 4.4 Ohmmeters 69 Summary 73 Review Questions 74	56
5	Components, Symbols, and Circuitry of Air-Conditioning Wiring Diagrams Objectives 76 Key Terms 76 Introduction 77 5.1 Loads 77 5.2 Contactors and Relays 82 5.3 Magnetic Starters 84 5.4 Switches 85 5.5 Safety Devices 88 5.6 Transformers 91 5.7 Schematic Diagrams 92 5.8 Pictorial Diagrams 93 5.9 Installation Diagrams 95 Summary 96 Review Questions 98	76
6	Reading Schematic Diagrams Objectives 100 Key Terms 100 Introduction 101 6.1 Schematic Diagram Design 102 6.2 Reading Basic Schematic Diagrams 106 6.3 Reading Advanced Schematic Diagrams 127 Summary 150 Review Questions 151	100
7	Alternating Current, Power Distribution, and Voltage Systems Objectives 153 Key Terms 153 Introduction 154 7.1 Basic Concepts of Alternating Current 154 7.2 Power Distribution 159 7.3 240-Volt-Single-Phase-60-Hertz Systems 160 7.4 Three-Phase Voltage Systems 162 7.5 240-Volt-Three-Phase-60-Hertz	153

Delta System 163 7.6 208-Volt Three-Phase 60-Hertz Wye System 164
 7.7 Higher-Voltage Systems 166 Summary 168 Review Questions 169

- 8 Basic Electric Motors 171**
 Objectives 171 Key Terms 171 Introduction 172 8.1 Magnetism 172 8.2 Basic Electric Motors 174 8.3 Types of Electric Motors 177 8.4 Shaded-Pole Motors 179 8.5 Capacitors 182 8.6 Split-Phase Motors 187 8.7 Permanent Split-Capacitor Motors 192 8.8 Capacitor-Start-Capacitor-Run Motors 195 8.9 Three-Phase Motors 197 8.10 Electronically Commutated Motors 199 8.11 Direct Current Brushless Motors 204 8.12 Hermetic Compressor Motors 205 8.13 Service Call Protocol 215 8.14 Service Calls 217 Summary 223 Review Questions 225 Practice Service Calls 229
- 9 Components for Electric Motors 233**
 Objectives 233 Key Terms 233 Introduction 234 9.1 Starting Relays for Single-Phase Motors 234 9.2 Current or Amperage Relays 235 9.3 Potential Relays 237 9.4 Solid-State Starting Relays and Devices 242 9.5 Motor Bearings 247 9.6 Motor Drives 250 9.7 Service Calls 253 Summary 258 Review Questions 260 Practice Service Calls 262
- 10 Contactors, Relays, and Overloads 265**
 Objectives 265 Key Terms 265 Introduction 266 10.1 Contactors 267 10.2 Relays 271 10.3 Overloads 277 10.4 Magnetic Starters 284 10.5 Push-Button Stations 287 10.6 Service Calls 288 Summary 292 Review Questions 294 Practice Service Calls 296
- 11 Thermostats, Pressure Switches, and Other Electric Control Devices 299**
 Objectives 299 Key Terms 299 Introduction 300 11.1 Transformers 301 11.2 Thermostats 303 11.3 Staging Thermostats 321 11.4 Programmable Thermostats 324 11.5 Communicating Thermostats 327 11.6 Wi-Fi Thermostats 330 11.7 Pressure Switches 333 11.8 Miscellaneous Electric Components 337 11.9 Service Calls 340 Summary 344 Review Questions 347 Practice Service Calls 350
- 12 Electronic Control Devices 354**
 Objectives 354 Key Terms 354 Introduction 355 12.1 Electronic System Components 356 12.2 Basic Electronic Control Fundamentals 361 12.3 Simple Electronic Temperature Control 362 12.4 One-Function Electronic Controls 363 12.5 Electronic Timers 363 12.6 Electronic Devices for Electric Motors 365 12.7 Electronic Motor Protection Devices 365 12.8 Heat Pump Electronic Modules 368 12.9 Electronic Control Modules for Residential Gas Furnaces 371 12.10 Oil Furnace Electronic Controls 375 12.11 Troubleshooting Electronic Controls 376 Summary 376 Review Questions 378
- 13 Heating Control Devices 380**
 Objectives 380 Key Terms 380 Introduction 381 13.1 Heating Fundamentals 383 13.2 Basic Heating Controls 385 13.3 Gas Heating Controls 392 13.4 Oil Heating Controls 404 13.5 Electric Heating Controls 410 13.6 Hydronic and Steam Controls 413 13.7 Service Calls 415 Summary 419 Review Questions 421 Practice Service Calls 423
- 14 Troubleshooting Electric Control Devices 426**
 Objectives 426 Key Terms 426 Introduction 427 14.1 Electric Motors 427 14.2 Contactors and Relays 429 14.3 Overloads 431 14.4 Thermostats 435

14.5 Pressure Switches 438 14.6 Transformers 439 14.7 Electric Heating Controls 440 14.8 Gas Heating Controls 442 14.9 Oil Heating Controls 453 14.10 Service Calls 456 Summary 462 Review Questions 464 Practice Service Calls 466

- 15 Residential Air-Conditioning Control Systems 473**
Objectives 473 Key Terms 473 Introduction 474 15.1 Residential Air-Conditioning Equipment 476 15.2 Basic Residential Control Circuitry 480 15.3 Packaged Air-Conditioning Control Systems 491 15.4 Split-System Air-Conditioning Control Systems 500 15.5 Heat Pump Control Systems 505 15.6 Heat Pump Sequence of Operation 513 15.7 Advanced Residential Control Systems 518 15.8 Mini-Split Control Systems 524 15.9 Field Wiring 527 15.10 Check, Test, and Start Procedures 536 15.11 Customer Relations 538 Summary 540 Review Questions 542
- 16 Installation of Heating, Cooling, and Refrigeration Systems 545**
Objectives 545 Key Terms 545 Introduction 546 16.1 Sizing Wire 546 16.2 Disconnect Switches 554 16.3 Fusible Load Centers 558 16.4 Breaker Panels 559 16.5 Distribution Centers 562 16.6 Installing Electrical Circuits for Refrigeration, Heating, and Air-Conditioning Equipment 564 Summary 569 Review Questions 570
- 17 Commercial and Industrial Air-Conditioning Control Systems 572**
Objectives 572 Key Terms 572 Introduction 573 17.1 Commercial and Industrial Heating and Air-Conditioning Equipment 574 17.2 Commercial and Industrial Control Circuitry 579 17.3 Commercial Condensing Unit 585 17.4 Commercial and Industrial Packaged Units 589 17.5 Air-Cooled Packaged Unit with Remote Condenser 591 17.6 Water-Cooled Packaged Units 595 17.7 Types of Total Commercial and Industrial Control Systems 596 17.8 Pneumatic Control Systems 600 17.9 Electronic Control Systems (Direct Digital Controls) 605 Summary 609 Review Questions 612
- 18 Troubleshooting Modern Refrigeration, Heating, and Air-Conditioning Control Circuitry and Systems 616**
Objectives 616 Key Terms 616 Introduction 617 18.1 Diagnosis of Electrical Components 618 18.2 Troubleshooting Tools 620 18.3 Troubleshooting with Electrical Meters 627 18.4 Using Troubleshooting Charts 636 18.5 Hopscotching: A Useful Tool for Troubleshooting 638 18.6 Troubleshooting Control Systems 650 18.7 Service Calls 653 Summary 659 Review Questions 661 Practice Service Calls 664
- Appendix A 668**
Appendix B 669
Glossary 670
Index 679

INDEX

A

- A (ampere), 28
- AC (alternating current). See Alternating current (AC)
- Advanced residential control systems, 518–524
 - advanced air-conditioning control systems, 518–519
 - zone control systems, 519–524
- Air-conditioning control systems, commercial and industrial. See Commercial and industrial air-conditioning control systems
- Air-conditioning control systems, residential. See Residential air-conditioning control systems
- Air-conditioning system controlled by a multistage thermostat, 131–135
- Air-conditioning system with lockout relay, 128–131
- Air-conditioning wiring diagrams, 76–97
 - contactors and relays, 82–84
 - installation diagrams, 95
 - introduction, 77
 - loads, 77–81
 - heaters, 80–81
 - motors, 78–80
 - signal lights, 81
 - solenoids, 80
 - magnetic starters, 84
 - pictorial diagrams, 93–95
 - safety devices, 88–91
 - schematic diagrams, 92–93
 - switches, 85–88
 - transformers, 91
- Air-cooled packaged units, 477
 - with remote condenser, 591–594
- Air supply sources for split-system residential systems, 503–505
- Alternating current (AC), 29, 153–159
 - alternators, 156–157
 - cycles and frequency, 155–156
 - effective voltage, 156
 - inductance and reactance, 158
 - introduction, 154–155
 - phase, 156
 - power, 159
 - voltage-current systems, 156
- Alternators, 156–157
- Aluminum ladders conduct shock, 6
- American Wire Gauge (AWG), 547
- Ammeters, 64–67
 - clamp-on, 57
- Amperage relays, 235–237
- Ampere (A), 28
- Analog meters, 60
- Anticipators, 312
- Anti-short-cycling circuitry, 583–585
- Anti-short-cycling timer, 363–365
- Applications
 - contactors, 267
 - parallel circuits, 47–48
 - programmable thermostats, 325–326
 - relays, 272–275
 - series circuits, 43–45
 - series-parallel circuits, 52–53
 - thermostats, 303–304
- Arc flashes, 7–8
- Atomic theory, 21–23
- Atoms, 21
- AWG (American Wire Gauge), 547

B

- Back electromotive force, 235
- Balance point, 139
- Ball bearings, 248

- Basic electricity, 20–37
 - atomic theory, 21–23
 - calculating electric power, 36
 - conductors and insulators, 27
 - current flow, 29–30
 - electric potential, 27–29
 - electric power and energy, 31–33
 - flow of electrons, 24–27
 - electricity through chemical means, 25–26
 - electricity through magnetism, 26–27
 - static electricity, 24–25
 - introduction, 21
 - Ohm's law, 33–35
 - positive and negative charges, 23–24
 - resistance, 30–31
 - Basic residential control circuitry, 480–491
 - compressor control circuits, 481
 - condenser fan motor control circuits, 481–482
 - evaporator fan motor control circuits, 482–483
 - furnace controls, 484–487
 - heat pump controls, 487–491
 - safety control circuits, 483
 - Bearings, 247–249
 - Bimetal elements, 305–306
 - Blower motor circuitry, 582–583
 - Blower units, 576
 - Breaker panels, 558–562
 - construction, 560–561
 - installation, 561–562
 - Breakers, 558
 - Broken circuit, 41
 - Burns, 5
- C**
- Cad cell, 406–407
 - Cad cell oil burner primary controls, 406–408
 - Calculations
 - current, resistance, and voltage
 - parallel circuits, 49–51
 - series circuits, 46–47
 - electric power, 36
 - voltage drop, 552–554
 - Capacitive reactance, 158
 - Capacitors, 182–187
 - troubleshooting, 183–186
 - two types used in the industry, 182–183
 - Capacitor-start–capacitor-run motors,
 - 195–197
 - operation, 195
 - troubleshooting, 195–197
 - Capacitor-start motors, 191
 - Capacity control, 579
 - Capacitor-start–induction-run motor, 191
 - Cardiopulmonary resuscitation (CPR), 8
 - Check, test, and start procedures, 536–537
 - Chemical means, 25–26
 - Circuit breakers, 13
 - Circuit lockout procedures, 14–16
 - Circuit protection, 13–14
 - Circuits, electric, 40–53
 - basic concepts, 41–43
 - introduction, 41
 - parallel circuits, 47–51
 - applications, 47–48
 - calculations for current, resistance, and voltage, 49–51
 - characteristics, 48–49
 - safety controls, condensing unit, 589
 - series circuits, 43–47
 - applications, 43–45
 - calculations for current, resistance, and voltage, 46–47
 - characteristics, 45–46
 - series-parallel circuits, 51–53
 - applications, 52–53
 - Clamp-on ammeter, 57
 - Closed circuit, 41
 - Coils, 269–270
 - Combustion chamber, 120
 - Commercial and industrial air-conditioning control systems, 572–611
 - air-cooled packaged unit with remote condenser, 591–594
 - commercial and industrial control circuitry, 579–585
 - anti-short-cycling circuitry, 583–585
 - blower motor circuitry, 582–583
 - compressor motor controls, 580–581
 - condenser fan motor circuitry, 583
 - water chiller control circuitry, 581–582
 - water-cooled condenser interlocks, 583

- commercial and industrial heating and air-conditioning equipment, 574–579
 - blower units, 576
 - commercial and industrial condensing units, 575
 - commercial and industrial packaged units, 575–576
 - hot water boilers, 576–577
 - water chillers, 577–579
- commercial and industrial packaged units, 589–590
- commercial condensing unit, 585–589
 - circuit safety controls, 589
 - compressor circuits, 585–587
 - condenser fan motor circuits, 587–589
- electronic control systems (direct digital controls), 605–609
- introduction, 573–574
- pneumatic control systems, 600–605
- types of total commercial and industrial control systems, 596–600
- water-cooled packaged units, 595–596
- Commercial freezers, 116–118
- Commercial refrigeration system with pump-down cycle, 144–150
- Communicating thermostats, 327–330
- Compounds, 22
- Compressor circuits, 585–587
- Compressor control circuits, 481
- Compressor motor controls, 580–581
- Condenser fan motor circuits, 583
- Condenser fan motor control circuits, 481–48
- Condensing unit, 476, 500–503, 585–589
 - circuit safety controls, 589
 - commercial and industrial air-conditioning control systems, 585–589
 - circuit safety controls, 589
 - compressor circuits, 585–587
 - condenser fan motor circuits, 587–589
 - compressor circuits, 585–587
 - condenser fan motor circuits, 587–589
- Conductors, 4, 23, 27
- Construction
 - breaker panels, 560–561
 - electronically commutated motors (ECMs), 200–202
 - relays, 275–276
- Contactors, 82–84, 267–271, 429
 - applications, 267
 - coils, 269
 - contacts, 269
 - operation, 267–269
 - troubleshooting, 270–271
- Contacts, 269
- Continuity, 69
- Control circuit, 43
- Control circuitry, commercial and industrial air-conditioning control systems, 579–585. *See also* Commercial and industrial air-conditioning control systems
 - anti-short-cycling circuitry, 583–585
 - blower motor circuitry, 582–583
 - compressor motor controls, 580–581
 - condenser fan motor circuitry, 583
 - water chiller control circuitry, 581–582
 - water-cooled condenser interlocks, 583
- Control circuitry, residential air-conditioning systems, 480–491. *See also* Residential air-conditioning control systems
 - compressor control circuits, 481
 - condenser fan motor control circuits, 481–48
 - evaporator fan motor control circuits, 482–483
 - furnace controls, 484–487
 - heat pump controls, 487–491
 - safety control circuits, 483
- Control devices, electric. *See* Electric control devices
- Control devices, electronic. *See* Electronic control devices
- Control devices, heater. *See* Heating control devices
- Controlling elements of thermostats, 304–308
- Control loop, 597
- Control relay, 128
- Control wiring, 527, 532–535
- CPR (cardiopulmonary resuscitation), 8
- Current, 29
- Current flow, 29–30
- Current or amperage relays, 235–237
 - operation, 235–236
 - troubleshooting, 237
- Current overload, 282
- Current-sensing lockout relay (CSLR), 643

- Cut-in pressure, 335
- Cut-out pressure, 335
- Cycles, 155
- D**
- DC (direct current), 29, 154
 - brushless motors, 204–205
- De-energized, 83
- Defrost controls, 508–511
- Defrost cycle, 139
- Dehumidifiers, 107–108
- Delay-on-make and break timers, 363
- Delta system, 163–164
- Delta winding, 198
- Diagrams
 - air-conditioning. *See* Air-conditioning wiring diagrams
 - electrical wiring diagrams, 620–624
 - as troubleshooting tool, 620–624
 - factual diagrams, 95
 - fault isolation diagrams, 636
 - installation diagrams, 95
 - line diagrams, 93
 - pictorial diagrams, 93–95
 - schematic diagrams. *See* Schematic diagrams
 - wiring. *See* Wiring diagrams
- Differential (of a pressure switch), 335
- Digital meters, 60
- Digital thermostat, 308
- Diodes, 358
- Direct current (DC), 29, 154
 - brushless motors, 204–205
- Direct digital control systems, 605–609
- Direct drive, 250
- Disconnect switches, 85, 554–558
 - enclosures, 556
 - fusible and nonfusible switches, 557–558
- Distribution centers, 562–564
- Double insulated tools, 11
- E**
- ECM (electronically commutated motor) savings
 - green technology, 204
- Effective voltage, 156
- Electrical grounding, 9–12
- Electrical injuries, 3–8
- Electrical meters, 620
- Electrical resistance heater, 384
- Electrical safety, 1–17
 - circuit lockout procedures, 14–16
 - circuit protection, 13–14
 - electrical grounding, 9–12
 - electrical injuries, 3–8
 - guidelines, 16–17
 - introduction, 2–3
 - National Electrical Code (NEC), 8–9
 - safety devices, 88–91
 - shock victims, dealing with, 8
- Electrical shock, 3–6, 8
- Electrical wiring diagrams, 620–624
 - for air-conditioning, 76–97
 - contactors and relays, 82–84
 - installation diagrams, 95
 - introduction, 77
 - loads, 77–81
 - heaters, 80–81
 - motors, 78–80
 - signal lights, 81
 - solenoids, 80
 - magnetic starters, 84
 - pictorial diagrams, 93–95
 - safety devices, 88–91
 - schematic diagrams, 92–93
 - switches, 85–88
 - transformers, 91
 - Electric circuits, 40–53
 - basic concepts, 41–43
 - introduction, 41
 - parallel circuits, 47–51
 - applications, 47–48
 - calculations for current, resistance, and voltage, 49–51
 - characteristics, 48–49
 - series circuits, 43–47
 - applications, 43–45
 - calculations for current, resistance, and voltage, 46–47
 - characteristics, 45–46
 - series-parallel circuits, 51–53
 - applications, 52–53
 - Electric control devices
 - humidistats, 337
 - oil safety switches, 337–338

- pressure switches, 87–88, 333–337, 390–392
 - high-pressure switches, 334–335
 - low-pressure switches, 335
 - notations and terms, 335–336
 - troubleshooting, 336–337
 - solenoid valves, 339–340
 - thermostats. *See* Thermostats
 - time clocks, 339
 - time-delay relays, 338–339
 - troubleshooting, 426–463
- Electric energy, 32**
- Electric heating controls, 410–412**
- Electricity, basic concepts of, 20–37**
- atomic theory, 21–23
 - calculating electric power, 36
 - conductors and insulators, 27
 - current flow, 29–30
 - electric potential, 27–29
 - electric power and energy, 31–33
 - flow of electrons, 24–27
 - electricity through chemical means, 25–26
 - electricity through magnetism, 26–27
 - static electricity, 24–25
 - introduction, 21
 - Ohm's law, 33–35
 - positive and negative charges, 23–24
 - resistance, 30–31
- Electric meters, 56–73, 620**
- ammeters, 64–67
 - basic principles, 58–59
 - differences among meters, 60–63
 - introduction, 57–58
 - ohmmeters, 69–73
 - voltmeters, 67–69
- Electric motors, basic, 78–80, 171–224**
- capacitors, 182–187
 - troubleshooting, 183–186
 - two types used in the industry, 182–183
 - capacitor-start–capacitor-run motors, 195–197
 - operation, 195
 - troubleshooting, 195–197
 - direct current brushless motors, 204–205
 - electronically commutated motors (ECMs), 199–204
 - construction, 200–202
 - operation, 202–203
 - troubleshooting, 203
 - hermetic compressor motors, 205–215
 - operation, 206–207
 - terminal identification, 207–208
 - troubleshooting, 208–215
 - introduction, 172, 174–176
 - loads, 78–80, 427
 - magnetism, 172–174
 - induced magnetism, 173–174
 - magnetic field, 173
 - permanent split-capacitor motors, 192–195
 - operation, 194
 - troubleshooting, 194–195
 - service calls, 215–223
 - examples, 217–223
 - protocol, 215–217
 - shaded-pole motors, 179–182
 - operation, 180–181
 - reversing, 181
 - troubleshooting, 181–182
 - split-phase motors, 187–192
 - capacitor-start–induction-run motor, 191
 - enclosed type, 192
 - open type, 191–192
 - operation, 189–190
 - resistance-start–induction-run motor, 187–189
 - troubleshooting, 190
 - three-phase motors, 197–199
 - operation, 197–198
 - troubleshooting, 198–199
 - types of, 177–179
 - motor dimensions, 179
 - motor speed, 177
 - motor strength, 177
 - open and enclosed motors, 178–179
- Electric motors, components of, 233–259**
- bearings, 247–249
 - ball bearings, 248
 - sleeve bearings, 249
 - current or amperage relays, 235–237
 - operation, 235–236
 - troubleshooting, 237
 - drives, 250–253
 - direct drive, 250
 - V-belt, 251–253
 - introduction, 234

- Electric motors, components of (*continued*)
 - potential relays, 237–241
 - operation, 237–239
 - troubleshooting, 239–241
 - service calls, 253–258
 - solid-state starting relays and devices, 242–247
 - operation, 246–247
 - troubleshooting, 247
 - starting relays for single-phase motors, 234–235
 - Electric potential, 27–29
 - Electric power and energy, 31–33
 - Electric pressure, 28
 - Electrodes, 25
 - Electrolytes, 25
 - Electromagnet, 173
 - Electromotive force, 3, 28
 - Electronically commutated motors (ECMs), 199–204
 - construction, 200–202
 - operation, 202–203
 - troubleshooting, 203
 - Electronic control devices, 354–377
 - basic electronic control fundamentals, 361–362
 - electronic control modules for residential gas furnaces, 371–374
 - electronic devices for electric motors, 365
 - electronic motor protection devices, 365–367
 - multifunction electronic motor protectors, 367
 - overload protection, 366
 - phase reversal protector, 367
 - single-phase protection, 367
 - electronic system components, 356–360
 - diodes and rectifiers, 358–359
 - LEDs, 360
 - semiconductors, 357–358
 - thermistors, 360
 - transistors, 359
 - triacs, 360
 - electronic timers, 363–365
 - anti-short-cycling timer, 363–365
 - delay-on-make and break timers, 363
 - heat pump electronic modules, 368–370
 - introduction, 355–356
 - oil furnace electronic controls, 375
 - one-function electronic controls, 363
 - simple electronic temperature control, 362
 - troubleshooting electronic controls, 376
 - Electronic control systems, 605–609
 - Electronic elements, 307–308
 - Electronic gas furnace control modules, 371
 - Electronic modules, 356
 - Electronic motor overloads, 366
 - Electronic motor protection devices, 365–367
 - multifunction electronic motor protectors, 367
 - overload protection, 366
 - phase reversal protector, 367
 - single-phase protection, 367
 - Electronic self-diagnostic feature, 627
 - Electronic system components, 356–360
 - diodes and rectifiers, 358–359
 - LEDs, 360
 - semiconductors, 357–358
 - thermistors, 360
 - transistors, 359
 - triacs, 360
 - Electronic timers, 363–365
 - anti-short-cycling timer, 363–365
 - delay-on-make and break timers, 363
 - Electrons, 21–22
 - flow of, 24–27
 - Elements, 21
 - Enclosed motors, 178–179
 - Energized, 83
 - Energy efficiency ratings
 - green technology, 476
 - Energy-efficient motors
 - green technology, 178
 - Evaporator fan motor control circuits, 482–483
- ## F
- Factory-installed wiring, 527
 - Factual diagrams, 95
 - Fan-coil unit, 479
 - Fan controls, 385–389
 - Fan switches, 386
 - Fault isolation diagram, 636
 - Field of force, 28
 - Field wiring, 527–535
 - control wiring, 532–535
 - power wiring, 527–530
 - wire and fuse sizing, 530–532
 - Flux, 173
 - Free electrons, 23

Freezers, commercial, 116–118

Frequency, 155–156

Full-load amperage (FLA), 235

Furnace controls, 484–487

Fuses, 13, 89, 277, 557–559

Fusible and nonfusible switches, 557–558

Fusible disconnect switch, 557

Fusible load centers, 558–559

G

Gas furnaces, 118

with standing pilot, 118–122

Gas heat electric air-conditioning packaged unit control system, 492–498

Gas heating controls, 392–404

direct ignition burner control system, 398–400

integrated furnace control boards, 400–404

intermittent pilot burner control system, 395–398

standing pilot burner control system, 392–395

Gas packs, 477

Gas valves, 392

Green technology

ECM (electronically commutated motor) savings, 204

energy efficiency ratings, 476

energy-efficient motors, 178

hybrid heat pump system, 507

mercury disposal, 320

multistage equipment, 321

PCBs (polychlorinated biphenyls), 187

programmable thermostats, 327

variable-speed compressors, 206

zoned air-conditioning systems, 522

Ground, 9

Ground fault circuit interrupter (GFCI), 11

Grounding adapter, 10

H

Heater, 80–81

Heater loads, 80–81

Heating anticipators, 312

Heating control devices, 380–420

basic heating controls, 385–392

fan controls, 385–389

limit switches, 389–390

pressure switches, 390–392

electric heating controls, 410–412

gas heating controls, 392–404

direct ignition burner control system, 398–400

integrated furnace control boards, 400–404

intermittent pilot burner control system, 395–398

standing pilot burner control system, 392–395

heating fundamentals, 383–385

hydronic and steam controls, 413–414

introduction, 381–383

oil heating controls, 404–410

cad cell oil burner primary controls, 406–408

stack switch oil burner primary controls, 408–410

service calls, 415–419

Heating fundamentals, 383–385

Heat pump, 135, 323–324, 477

control module, 368

control systems, 487–491, 505–513

defrost controls, 508–511

heat pump electrical components, 508

reversing valves, 508

supplementary heat, 511–513

electrical components, 508

electronic module, 368–370

hybrid heat pump system, 507

sequence of operation, 513–518

with solid-state defrost board, 135–144

Hermetic compressor motors, 205–215

operation, 206–207

terminal identification, 207–208

troubleshooting, 208–215

Higher-voltage systems

advantages, 166

disadvantages, 166

277/480-volt system, 166–167

High-pressure switches, 334–335

Hopscotching, 638–650

Hot surface ignition, 398

Hot water boilers, 576–577

HSPF (Heating Seasonal Performance Factor), 476

Humidistats, 337

Hybrid heat pump system

green technology, 507

Hydronic and steam controls, 413–414

- I**
- Ignition module, 371, 396
 - Impedance, 158
 - Induced magnetism, 173–174
 - Inductance, 158
 - Inductive loads, 269, 277
 - Inductive reactance, 158
 - Industrial air conditioning and control systems.
 - See Commercial and industrial air-conditioning control systems
 - Injuries, electrical, 3–8. See also Safety
 - Installation and service instructions, 625
 - Installation diagrams, 95
 - Installation of heating, cooling, and refrigeration systems, 545–569
 - breaker panels, 559–562
 - construction, 560–561
 - installation, 561–562
 - disconnect switches, 554–558
 - enclosures, 556
 - fusible and nonfusible switches, 557–558
 - distribution centers, 562–564
 - fusible load centers, 558–559
 - installing electrical circuits for refrigeration, heating, and air-conditioning equipment, 564–569
 - introduction, 546
 - sizing wire, 546–554
 - calculating voltage drop, 552–554
 - factors to consider in wiring, 547
 - voltage drop, 547–552
 - wire size, 547
 - wire-sizing charts, 552
 - Insulators, 27
 - Interlock, 581
 - Internal compressor overloads, 280
- K**
- Kilowatthours (kWh), 32
- L**
- Label, 93
 - Ladders, 6
 - Law of electric charges, 23
 - Light commercial air-conditioning control system with a control relay, 127–128
 - Light-emitting diode (LED), 360
 - Limit switch, 120, 389–390
 - Line break and pilot duty overloads, 277–283
 - Line diagram, 93
 - Line-voltage control system, 107
 - Line-voltage thermostat, 304, 308–309
 - Live electrical circuit, 2
 - Loads, 77–81
 - heaters, 80–81
 - motors, 78–80
 - signal lights, 81
 - solenoids, 80
 - Loads, resistive, 269, 277
 - Locked rotor amperage (LRA), 235
 - Lockout relay, 128
 - Low-pressure switch, 335
 - Low-voltage control system, 104, 118–120
 - Low-voltage thermostats, 304, 309–316
- M**
- Made circuit, 41
 - Magnetic field, 58, 173
 - Magnetic overload, 89, 282
 - Magnetic relay, 235
 - Magnetic starters, 84, 284–287
 - troubleshooting, 286–287
 - types of magnetic starter overloads and their operation, 286
 - Magnetism, 26–27, 172–174
 - induced magnetism, 173–174
 - magnetic field, 173
 - Matter, 21
 - Measurable resistance, 69
 - Mechanical linkage, 270
 - Mercury disposal
 - green technology, 320
 - Meters, electric, 56–73, 620
 - ammeters, 64–67
 - basic principles, 58–59
 - differences among meters, 60–63
 - introduction, 57–58
 - ohmmeters, 69–73
 - voltmeters, 67–69
 - Microfarad, 183
 - Mini-split control systems, 525–527
 - Molecules, 21

Motors. *See* Electric motors, basic; Electric motors, components of

Multifunction electronic motor protectors, 367

Multistage equipment
green technology, 321

Multistage thermostat, 131

N

National Electrical Code (NEC), 8–9, 546

National Fire Protection Association, 8

Negative and positive charges, 23–24

Neutrons, 22

Nonconductive ladders, 6

Nonfusible disconnect switch, 557

Noninductive loads, 277

Normally closed contacts, 83

“Normally,” meaning of, 83

Normally open contacts, 83

Nucleus, 21

O

Ohmmeters, 60, 69–73

Ohm’s law, 33–35

Ohm (Ω), 28

Oil furnace electronic controls, 375

Oil heating controls, 404–410
cad cell oil burner primary controls, 406–408
stack switch oil burner primary controls, 408–410

Oil safety switch, 337–338

One-function electronic controls, 363

Open and enclosed motors, 178–179

Open circuit, 41

Opens (open circuits), 69

Overloads, 277–284
fuses, 277
line break and pilot duty overloads, 277–283
protection, 366
troubleshooting, 284

P

Packaged air-conditioning control systems,
491–500
commercial and industrial, 589–590
gas heat electric air-conditioning packaged unit
control system, 492–498
packaged air-conditioning unit control systems,
492

packaged heat pump control systems,
498–500

Packaged air-conditioning equipment, 122–127,
476–479

Packaged units, 476

Parallel circuits, 47–51
applications, 47–48
calculations for current, resistance, and voltage,
49–51
characteristics, 48–49

PCBs (polychlorinated biphenyls)
green technology, 187

Peak voltage, 156

Permanent magnet, 173

Permanent split-capacitor motors, 192–195
operation, 194
troubleshooting, 194–195

Phase, 156

Phase reversal protector, 367

Pictorial diagrams, 93–95

Pilot, 381

Pilot assembly, 396

Pilot duty device, 89

Pilot duty overload, 278, 281–283

Plugs, 10

Pneumatic control systems, 600–605

Pole, 83

Polychlorinated biphenyls (PCBs)
Green technology, 187

Positive and negative charges, 23–24

Potential difference, 28

Potential relays, 237–241
operation, 237–239
troubleshooting, 239–241

Power, 159

Power circuits, 47

Power distribution, 159–160

Power factor, 31, 159

Power wiring, 527–530

Pressure elements, 306–307

Pressure switches, 87–88, 333–337, 390–392,
438
high-pressure switches, 334–335
low-pressure switches, 335
notations and terms, 335–336
troubleshooting, 336–337

- Primary control, 405
 - Programmable thermostats, 324–327
 - applications, 325–326
 - green technology, 327
 - installation, 326–327
 - programming the electronic digital programmable thermostat, 327
 - Protons, 22
 - Pump, heat. *See* Heat pump
 - Pump-down control system, 144
 - Push-button stations, 287–288
 - Push-button switch, 85
- R**
- Range (of a control), 335
 - Reactance, 158
 - Reactance, capacitive, 158
 - Reading advanced schematic diagrams, 127–150.
 - See also* Schematic diagrams, reading
 - Reading basic schematic diagrams, 106–127. *See also* Schematic diagrams, reading
 - Rectifiers, 358–359
 - Relays, 82–84, 271–277, 429
 - applications, 272–275
 - construction, 275–276
 - operation, 271–272
 - troubleshooting, 277
 - Residential air-conditioning control systems, 473–541
 - advanced residential control systems, 518–524
 - advanced air-conditioning control systems, 518–519
 - zone control systems, 519–524
 - basic residential control circuitry, 480–491
 - compressor control circuits, 481
 - condenser fan motor control circuits, 481–48
 - evaporator fan motor control circuits, 482–483
 - furnace controls, 484–487
 - heat pump controls, 487–491
 - safety control circuits, 483
 - check, test, and start procedures, 536–537
 - customer relations, 538–540
 - equipment, 476–480
 - packaged air-conditioning equipment, 476–479
 - split air-conditioning systems, 479–480
 - field wiring, 527–535
 - control wiring, 532–535
 - power wiring, 527–530
 - wire and fuse sizing, 530–532
 - heat pump control systems, 505–513
 - defrost controls, 508–511
 - heat pump electrical components, 508
 - reversing valves, 508
 - supplementary heat, 511–513
 - heat pump sequence of operation, 513–518
 - introduction, 474–475
 - mini-split control systems, 525–527
 - packaged air-conditioning control systems, 491–500
 - gas heat electric air-conditioning packaged unit control system, 492–498
 - package air-conditioning unit control systems, 492
 - packaged heat pump control systems, 498–500
 - split-system air-conditioning control systems, 500–505
 - air supply sources for split-system residential systems, 503–505
 - basic condensing units, 500–503
 - Residential gas furnaces, electronic control modules for, 371–374
 - Resistance, 30–31
 - measurable, 69
 - Resistance-start-induction-run motor, 187–189
 - Resistive load, 269, 277
 - Reversing shaded-pole motors, 181
 - Reversing valve, 135, 505, 508
 - Rotors, 174
 - Running capacitor, 183
- S**
- Safety, electrical, 1–17
 - circuit lockout procedures, 14–16
 - circuit protection, 13–14
 - electrical grounding, 9–12
 - electrical injuries, 3–8
 - guidelines, 16–17
 - introduction, 2–3
 - National Electrical Code (NEC), 8–9
 - safety devices, 88–91
 - shock victims, dealing with, 8

- Safety control circuits, 483
- Schematic diagrams, 92–93
 - design, 102–106
 - reading, 100–150
 - advanced schematic diagrams, 127–150
 - air-conditioning system controlled by a multistage thermostat, 131–135
 - air-conditioning system with lockout relay, 128–131
 - basic schematic diagrams, 106–127
 - commercial freezer, 116–118
 - commercial refrigeration system with pump-down cycle, 144–150
 - dehumidifier, 107–108
 - gas furnace with standing pilot, 118–122
 - heat pump with solid-state defrost board, 135–144
 - introduction, 101–102
 - light commercial air-conditioning control system with a control relay, 127–128
 - packaged air-conditioning unit, 122–127
 - reading advanced schematic diagrams, 127–150
 - reading basic schematic diagrams, 106–127
 - schematic diagram design, 102–106
 - simple window air conditioner, 108–113
 - walk-in cooler, 113–116
- Seasonal energy efficiency ratio (SEER), 32, 476
- Semiconductors, 357–358
- Sequencer, 410
- Series circuits, 43–47
 - applications, 43–45
 - calculations for current, resistance, and voltage, 46–47
 - characteristics, 45–46
- Series-parallel circuits, 51–53
 - applications, 52–53
- Service calls, 288–292
 - electric motors, components of, 253–258
 - examples, 217–223
 - heating control devices, 415–419
 - protocol, 215–217
 - thermostats, 340–344
- Set point, 108
- Shaded-pole motors, 179–182
 - operation, 180–181
 - reversing, 181
 - troubleshooting, 181–182
- Shock victims, dealing with, 8
- Short cycles, 128
- Shorts (short circuits), 69
- Signal lights, 81
- Simple electronic temperature control, 362
- Simple window air conditioner, 108–113
- Sine wave, 154
- Single-phase current, 156
- Single-phase protection, 367
- Sizing wire, 546–554
 - calculating voltage drop, 552–554
 - factors to consider in wiring, 547
 - voltage drop, 547–552
 - wire size, 547
 - wire-sizing charts, 552
- Sleeve bearings, 249
- Snap action, 305
- Solenoid, 80
- Solenoid loads, 80
- Solenoid valves, 339–340
- Solid state, 357
- Solid-state starting relays and devices, 242–247
 - operation, 246–247
 - troubleshooting, 247
- Spark ignition, 398
- Speed of electric motors, 177
- Split air-conditioning systems, 476, 479–480
- Split-phase motors, 187–192
 - capacitor-start-induction-run motor, 191
 - enclosed type, 192
 - open type, 191–192
 - operation, 189–190
 - resistance-start-induction-run motor, 187–189
 - troubleshooting, 190
- Split system, 475
- Split-system air-conditioning control systems, 500–505
 - air supply sources for split-system residential systems, 503–505
 - basic condensing units, 500–503
- Squirrel cage rotor, 176

- Stack switch, 406
 - Stack switch oil burner primary controls, 408–410
 - Staging thermostats, 321–324
 - heat pumps, 323–324
 - operation and types, 322–323
 - staging system, 321–322
 - Starting capacitors, 182
 - Starting relay, 234
 - for single-phase motors, 234–235
 - Start procedure (check, test, and start), 536–537
 - Star winding, 198
 - Static electricity, 24–25
 - Stators, 174
 - Steam and hydronic controls, 413–414
 - Strength of electric motors, 177
 - Supplementary heat, 511–513
 - Switches, 85–88
 - Systems, voltage, 160–167
 - higher-voltage systems, 166–167
 - advantages, 166
 - disadvantages, 166
 - 277/480-volt system, 166–167
 - three-phase voltage systems, 162–163
 - 240-volt-single-phase-60-Hertz systems, 160–162
 - 240-volt-three-phase-60-Hertz delta system, 163–164
 - 208-volt-three-phase-60-Hertz wye system, 164–166
- T**
- Terminal identification, in hermetic compressor motors, 207–208
 - Test procedure (check, test, and start procedures), 536–537
 - Thermal overload, 89
 - Thermistors, 357, 360
 - Thermocouple, 392–394
 - Thermostats, 87, 303–320, 435
 - applications, 303–304
 - communicating thermostats, 327–330
 - controlling elements of thermostats, 304–308
 - installation, 316–319
 - line-voltage thermostats, 308–309
 - low-voltage thermostats, 309–316
 - miscellaneous electric components, 337–340
 - humidistats, 337
 - oil safety switch, 337–338
 - solenoid valves, 339–340
 - time clock, 339
 - time-delay relay, 338–339
 - pressure switches, 333–337
 - high-pressure switches, 334–335
 - low-pressure switches, 335
 - notations and terms, 335–336
 - troubleshooting, 336–337
 - programmable thermostats, 324–327
 - applications, 325–326
 - installation, 326–327
 - programming the electronic digital programmable thermostat, 327
 - service calls, 340–344
 - staging thermostats, 321–324
 - heat pumps, 323–324
 - operation and types, 322–323
 - staging system, 321–322
 - troubleshooting, 319–320
 - wi-fi thermostats, 330–333
- Three-phase current, 156
 - Three-phase motors, 197–199
 - operation, 197–198
 - troubleshooting, 198–199
 - Three-phase voltage systems, 162–163
 - Three-prong plug, 10
 - Throw, 85
 - Time clocks, 339
 - Time-delay relay, 338–339
 - Timers, delay-on-make and break, 363
 - Timers, electronic, 363–365
 - anti-short-cycling timer, 363–365
 - delay-on-make and break timers, 363
 - Torque, 172
 - Total commercial and industrial control systems, 596–600
 - Transformers, 91, 301–303
 - operation, 301–301
 - sizing, 302–303
 - troubleshooting, 303
 - Transistors, 359
 - Triacs, 360

- Troubleshooting, 426–463, 616–660
- capacitors, 183–186
 - capacitor-start-capacitor-run motors, 195–197
 - contactors, 270–271
 - contactors and relays, 429–431
 - coil, 430
 - contacts, 429–430
 - mechanical linkage, 430–431
 - control systems, 650–653
 - industrial systems, 652–653
 - residential systems, 652
 - current or amperage relays, 237
 - electrical components, 618–620
 - contactors and relays, 619–620
 - motors, 619
 - other electrical devices, 620
 - switches, 619
 - electrical meters, 627–636
 - electric heating controls, 440–442
 - electric motors, 427–429
 - electronically commutated motors (ECMs), 203
 - electronic controls, 376
 - gas heating controls, 442–453
 - direct ignition control systems, 449
 - gas valves, 443–446
 - integrated furnace control, 449–453
 - intermittent pilot systems, 446–448
 - hermetic compressor motors, 208–215
 - hopscotching: a useful tool for troubleshooting, 638–650
 - introduction, 427, 617–618
 - magnetic starters, 286–287
 - oil heating controls, 453–456
 - cad cell primary controls, 455–456
 - stack switch primary controls, 453–455
 - overloads, 284, 431–435
 - circuit breaker, 432
 - fuse, 431
 - internal overloads, 434–435
 - line voltage overload, 432
 - pilot duty overload, 432–434
 - permanent split-capacitor motors, 194–195
 - potential relays, 239–241
 - pressure switches, 336–337, 438–439
 - refrigeration, heating, and air-conditioning control circuitry and systems, 616–660
 - relays, 277
 - service calls, 456–462, 653–659
 - shaded-pole motors, 181–182
 - solid-state starting relays and devices, 247
 - split-phase motors, 190
 - thermostats, 319–320, 435–437
 - line-voltage thermostat, 436
 - low-voltage thermostat, 436–437
 - three-phase motors, 198–199
 - tools for, 620–627
 - electrical meters, 620
 - electrical wiring diagrams, 620–624
 - electronic self-diagnostic feature, 627
 - installation and service instructions, 625
 - troubleshooting charts, 625–627, 636–638
 - transformers, 439–440
 - Troubleshooting tree, 636
- V**
- Variable-speed compressors
 - green technology, 206
 - Varistor, 357
 - V-belt, 251
 - V-belt drive, 251–253
 - V-belt motors, 251–253
 - Voltage, 28
 - Voltage-current systems, 156
 - Voltage drop, 46
 - sizing wire, 547–552
 - Voltage spikes, 361
 - Voltage systems, 160–167
 - 208-volt-three-phase-60-Hertz wye system, 164–166
 - 240-volt-single-phase-60-Hertz systems, 160–162
 - 240-volt-three-phase-60-Hertz delta system, 163–164
 - higher-voltage systems, 166–167
 - advantages, 166
 - disadvantages, 166
 - 277/480-volt system, 166–167
 - three-phase voltage systems, 162–163
 - Voltmeters, 60, 67–69
 - Volt-ohm-milliammeters, 57
 - Volt (V), 28

W

- Walk-in cooler, 113–116
- Water chillers, 577–579
 - control circuitry, 581–582
- Water-cooled condenser interlocks, 583
- Water-cooled condensing units, 583
- Water-cooled packaged units, 477, 595–596
- Water source heat pump, 477–478
- Watts (W), 31
- Wi-fi thermostats, 330–333
- Window air conditioner, simple, 108–113
- Wire, sizing, 546–554
 - calculating voltage drop, 552–554
 - factors to consider in wiring, 547
 - voltage drop, 547–552
 - wire size, 547
 - wire-sizing charts, 552
- Wire and fuse sizing, 530–532
- Wiring, field, 527–535
 - control wiring, 532–535
 - power wiring, 527–530
 - wire and fuse sizing, 530–532

- Wiring diagrams, for air-conditioning, 76–97
 - contactors and relays, 82–84
 - installation diagrams, 95
 - introduction, 77
 - loads, 77–81
 - heaters, 80–81
 - motors, 78–80
 - signal lights, 81
 - solenoids, 80
 - magnetic starters, 84
 - pictorial diagrams, 93–95
 - safety devices, 88–91
 - schematic diagrams, 92–93
 - switches, 85–88
 - transformers, 91
- Wye system, 164

Z

- Zone control systems, 519–524
- Zoned air-conditioning systems
 - green technology, 522